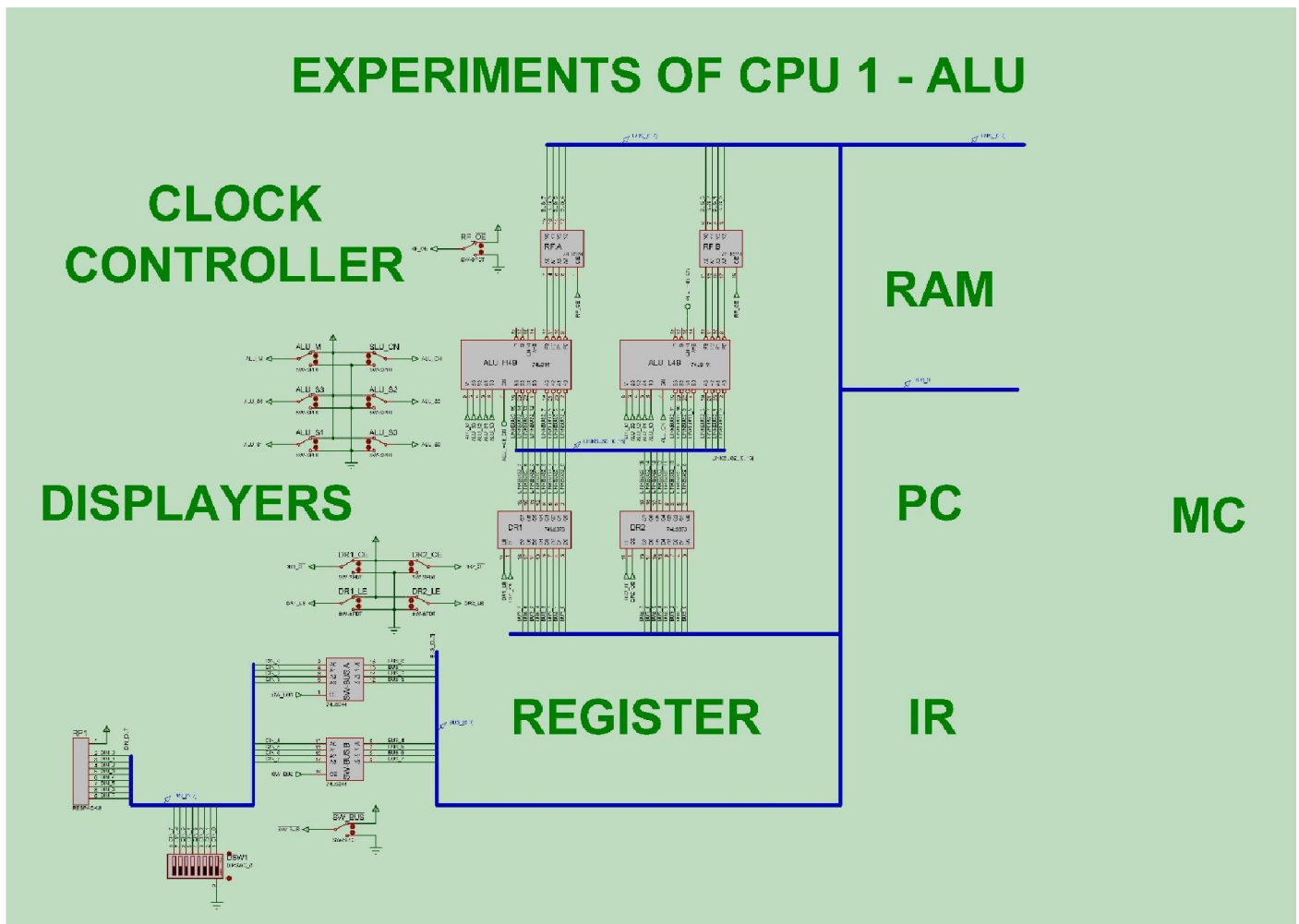


Laboratory Manual of Computer Organization and Architecture


EXPERIMENTS 1 – ALU

Circuit Diagram



Device List

74LS181: Arithmetic Logic Unit

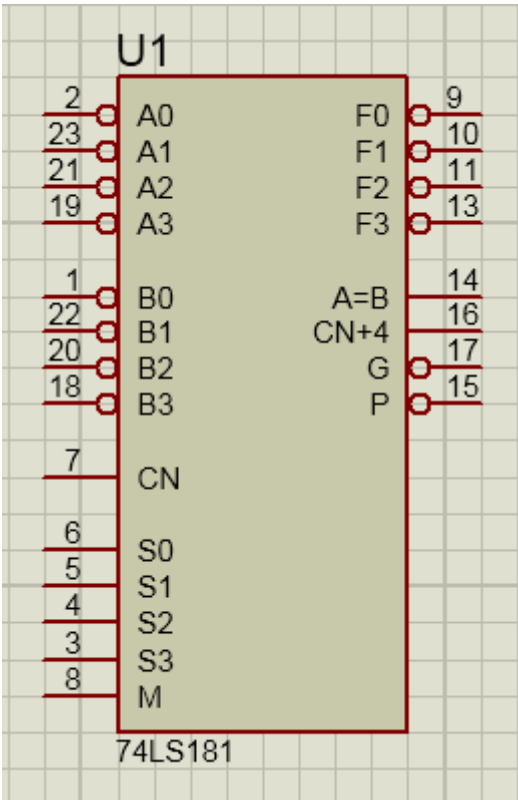


Function Table									
Mode Select Inputs				Active LOW Operands & F _n Outputs		Active HIGH Operands & F _n Outputs			
S3	S2	S1	S0	Logic (M = H)	Arithmetic** (M = L) (C _n = L)	Logic (M = H)	Arithmetic** (M = L) (C _n = H)		
L	L	L	L	\overline{A}	A minus 1	\overline{A}	A		
L	L	L	H	\overline{AB}	AB minus 1	$\overline{A + B}$	A + B		
L	L	H	L	$\overline{A + B}$	\overline{AB} minus 1	\overline{AB}	A + \overline{B}		
L	L	H	H	Logic 1	minus 1	Logic 0	minus 1		
L	H	L	L	$\overline{A + B}$	A plus (A + \overline{B})	\overline{AB}	A plus \overline{AB}		
L	H	L	H	\overline{B}	AB plus (A + \overline{B})	\overline{B}	(A + B) plus \overline{AB}		
L	H	H	L	$\overline{A \oplus B}$	A minus B minus 1	A \oplus B	A minus B minus 1		
L	H	H	H	A + \overline{B}	A + \overline{B}	\overline{AB}	AB minus 1		
H	L	L	L	\overline{AB}	A plus (A + B)	$\overline{A + B}$	A plus AB		
H	L	L	H	A \oplus B	A plus B	$\overline{A \oplus B}$	A plus B		
H	L	H	L	B	\overline{AB} plus (A + B)	B	(A + \overline{B}) plus AB		
H	L	H	H	A + B	A + B	AB	AB minus 1		
H	H	L	L	Logic 0	A plus A*	Logic 1	A plus A*		
H	H	L	H	\overline{AB}	AB plus A	A + \overline{B}	(A + B) plus A		
H	H	H	L	AB	\overline{AB} minus A	A + B	(A + \overline{B}) plus A		
H	H	H	H	A	A	A	A minus 1		

*Each bit is shifted to the next most significant position.

**Arithmetic operations expressed in 2s complement notation.

 74LS244: Octal Buffers/Line Drivers with Tristate Outputs



Function Table

Inputs		Output
\overline{G}	A	Y
L	L	L
L	H	H
H	X	Z


L = LOW Logic Level

H = HIGH Logic Level

X = Either LOW or HIGH Logic Level

Z = High Impedance

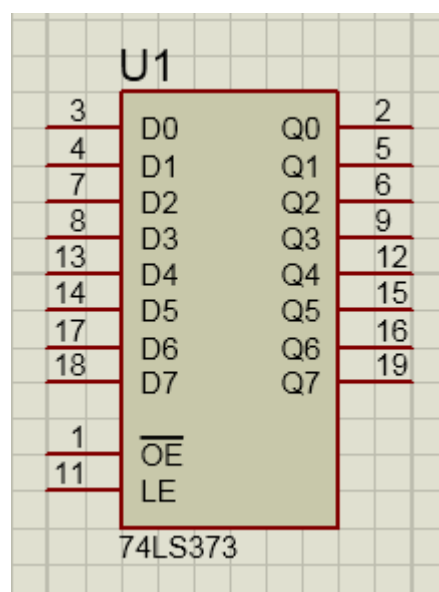74LS373: Octal D-Type Transparent Latches with Tristate Outputs





SN54/74LS373 • SN54/74LS374

TRUTH TABLE



LS373			
D _n	LE	$\overline{\text{OE}}$	O _n
H	H	L	H
L	H	L	L
X	L	L	Q ₀
X	X	H	Z*

H = HIGH Voltage Level
L = LOW Voltage Level
X = Immaterial
Z = High Impedance


LS374			
D _n	LE	$\overline{\text{OE}}$	O _n
H		L	H
L		L	L
X	X	H	Z*

* Note: Contents of flip-flops unaffected by the state of the Output Enable input ($\overline{\text{OE}}$).

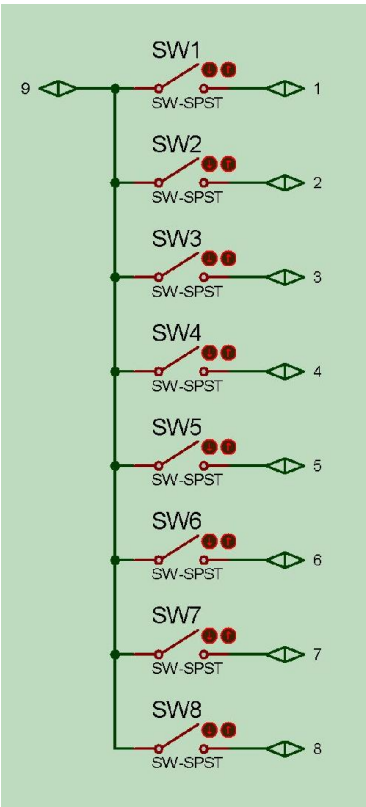 DIPSWC_8: Interactive DIP Switch 8 Common elements



 RESPACK-8: 8 way resistor pack with common



SW-SPDT: Interactive SPDT(Single-Pole Double-Throw) Switch

 


Table of Experiment Data Record

S3 S2 S1 S0	Data1	Data2	Arithmetic Operation (M = 0)		Logic Operation (M = 1)
			CN = 1 (No Carry)	CN = 0 (Carry)	
0 0 0 0	0AAH	55H			
0 0 0 1	0AAH	55H			
0 0 1 0	0AAH	55H			
0 0 1 1	0AAH	55H			
0 1 0 0	0FFH	01H			
0 1 0 1	0FFH	01H			
0 1 1 0	0FFH	01H			
0 1 1 1	0FFH	01H			
1 0 0 0	0FFH	0FFH			
1 0 0 1	0FFH	0FFH			
1 0 1 0	0FFH	0FFH			
1 0 1 1	0FFH	0FFH			
1 1 0 0	55H	01H			
1 1 0 1	55H	01H			
1 1 1 0	55H	01H			
1 1 1 1	55H	01H			

Steps of the Experiment

- (1) Reset all the enabling pins of 74LS181. Set all the enabling pins of other devices;
- (2) Lock data 0AAH to DR1 and data 55H to DR2. Disable the output of SW-BUS;
- (3) Set the enabling pins $S_3S_2S_1S_0$ into 0000. Reset the enabling pin M and set the enabling pin CN. Record the output data of 74LS181;
- (4) Keep the state of enabling pins $S_3S_2S_1S_0$ and the enabling pin M. Reset the enabling pin CN. Record the output data of 74LS181;
- (5) Keep the state of enabling pins $S_3S_2S_1S_0$. Set the enabling pin M. Record the output data of 74LS181;
- (6) Set the enabling pins $S_3S_2S_1S_0$ into the next state and redo the step (2) to (5).

EXPERIMENTS OF CPU 1 - ALU

CLOCK
CONTROLLER

RAM

DISPLAYERS

PC

MC

REGISTER

IR

